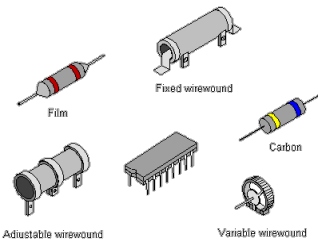


# Unit 10 Resistors



Jan 29-10:29 AM

## Resistance

SLIDE FROM UNIT  
5

- Denoted by "R"
- Oppose to the flow of the current (goes against)
- measured in ohm ( $\Omega$ )
- measured by an ohmmeter
- due to not wanting to get rid of valence e<sup>-</sup> or the fact e<sup>-</sup> are bumping into to many other electrons
- depends on the size, type and temperature of material
- resistance causes heat in the conductor

$$R = \frac{V}{I}$$

↑ V cause ↑ R

↓ V cause ↓ R

↑ I cause ↓ R

↓ I cause ↑ R

Feb 1-11:29 AM

- depends on the size, type and temperature of material

If length increases then so does resistance

Ex} A 60 ft #22 insulated copperwire has resistance of 1 then a 120 ft wire has approximately  $2\Omega$

if you double length you double resistance

Length is directly proportional to resistance of conductor

Larger diameter the less resistance

↓ Gauge

Temperature has different results depending on the material

Most cases: Increase temperature causes increase of resistance

-known as positive temperature coefficient



Negative temperature coefficient: means resistance decreases as temperature increases (or opposite)



If resistance doesn't change when material changes temperature then this is known as "constant temperature coefficient" — —

Feb 19-10:48 PM

## Resistance Wire

- used to produce heat for heating electricity


- Nichrome wire is the most popular resistance wire.

\*high-resistance

\* made of nickel and chromium

- used in heating elements in stoves, dryers, toasters and other heating appliances

- when a voltage is applied to the heating element, the high resistance of the wire converts most of the electrical energy into heat energy.

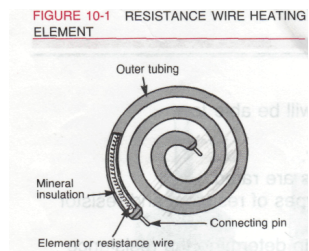

Feb 10-4:22 PM

## Resistors

-A resistor is an electrical component added to a circuit to lower the current flow or reduce the voltage

-A resistor is rated in 3 ways:

1) Resistance

-measured in ohms ( $\Omega$ )


2) Can't measure an exact number of ohms of resistors; therefore, most resistors carry a percentage tolerance or accuracy rating.

3) Amount of power the resistor can safely handle in watts (W)

- resistors carry current that produces heat

-

FIGURE 10-3 RESISTOR RATINGS

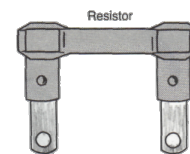

Typical rating  
 1. 500  $\Omega$  resistance  
 2.  $\pm$  5% tolerance  
 3. 10 W

Feb 10-5:03 PM

1 OHM is the amount of resistance that will allow 1 ampere of current to flow in a circuit to which 1 voltage is applied.

If 1 Volt causes 1 ampere of current in a circuit then the resistance of the circuit is 1 ohm.

$$R = \frac{V}{I}$$

Feb 19-10:32 PM

OHM

 $1\ \Omega$  $1000\ \Omega = 1\ \text{k}\Omega$  $1\ 000\ 000\ \Omega = 1\ \text{M}\Omega$ 

Prefix	Analog value
p (pico)	$10^{-12}$
n (nano)	$10^{-9}$
$\mu$ (micro)	$10^{-6}$
m (milli)	$10^{-3}$
☺ k ( <u>kilo</u> )	$10^3$ (1000)
☺ M ( <u>mega</u> )	$10^6$ (1,000,000)
G ( <u>Giga</u> )	$10^9$ (1,000,000,000)
T (Tera)	$10^{12}$ (1,000,000,000,000)

Feb 19-10:37 PM

## Types of Resistors

Two ways to classify resistor:


- Classified according to their construction
- Classified according to their function

Feb 19-12:02 PM

## Construction

### Wirewound Resistor

- high-resistance wire wrapped around an insulated cylinder
- rate of resistance is related to length of wire used
- most expensive to manufacture
- used in circuits with high currents or require accurate resistance  
lots of power

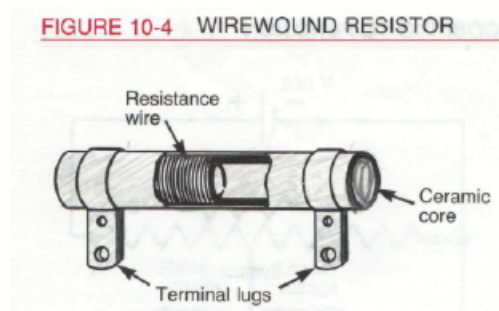


Feb 19-8:58 PM

## Construction
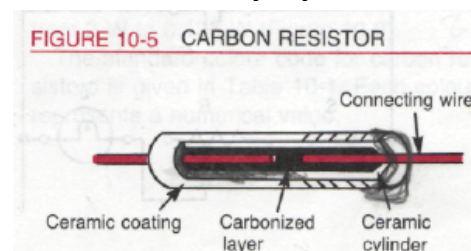
### Carbon Resistor

- made from consisting of carbon and a filler material.
- Resistance is determined by the amount of carbon used in making the resistor
- Cheapest to manufacture (so most common used)
- cannot handle large currents
- actual resistance can vary by 20% from actual rate




P  
399  
14

Feb 19-8:58 PM

**function**Fixed Resistor


- Functions at one non-variable ohmic value

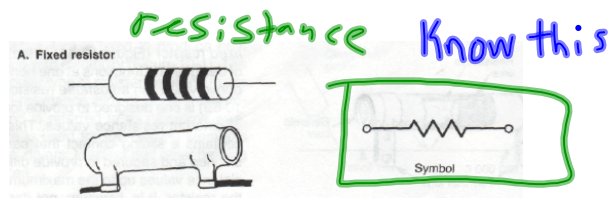

Feb 19-8:58 PM

**function**Adjustable Resistor

- designed to provide for a range of different resistance values
- has a sliding contact that can be positioned and secured to provide different resistance values (up to the maximum value of the resistor)
- not designed for continuous adjustments

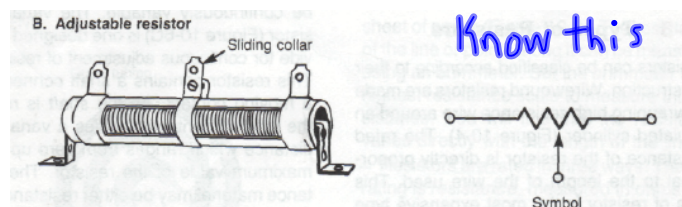


Feb 19-8:58 PM

## function

[http://wn.com/variable\\_resistor#/videos](http://wn.com/variable_resistor#/videos)
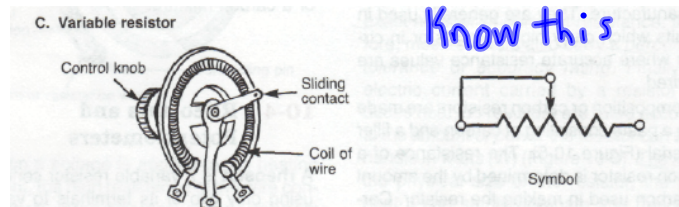
### Variable Resistor

- designed for continuous adjustments of resistance
- Shaft connected to moving contact
- shaft rotates and the sliding contact provide a variable resistance from 0 to maximum



A resistor may have one or more fixed tapping points so that the resistance can be changed by moving the connecting wires to different terminals. Some wirewound power resistors have a tapping point that can slide along the resistance element, allowing a larger or smaller part of the resistance to be used.


Feb 19-8:58 PM

## **Rheostats & Potentiometers**

<http://vimeo.com/25186895>

### Rheostat:

- is a variable resistor
- uses only 2 of its terminals to vary the resistance
- Ex) Dash light dimmer in car

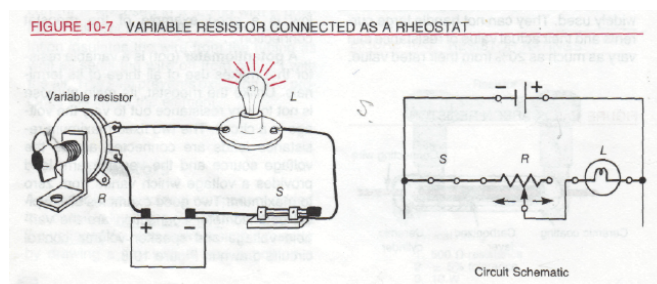


Feb 19-9:13 PM

## Rheostats & Potentiometers

### Potentiometer:

- is a variable resistor
- uses all 3 of its terminals to vary the voltage
- the 2 fixed maximum resistance leads are connected across the voltage which varies from 0 to maximum.
- Ex) Speaker volume

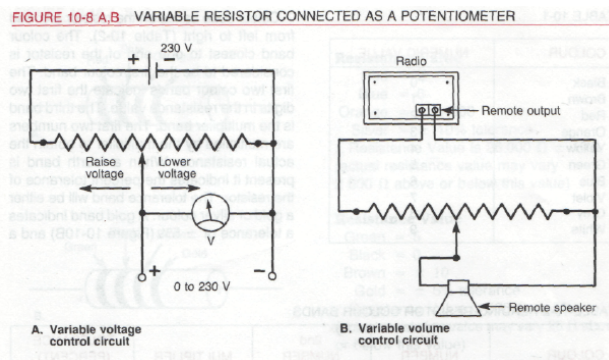

Feb 19-11:15 PM


## Resistor Colour Code

- Carbon resistors use bands of colour to represent resistance value and tolerance.
- Colour bands makes it easier to read regardless where it is located in the circuit.

Feb 19-11:18 PM



- Power rate is determined by the size  
 -From 2 W to 0.125 W

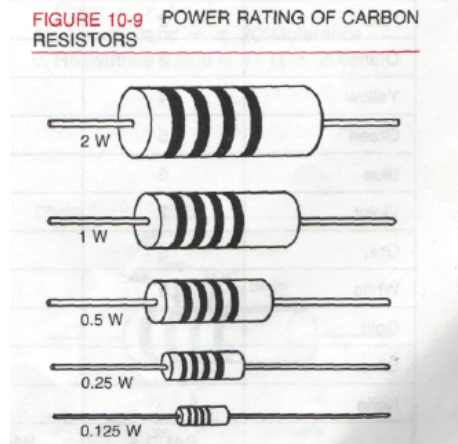

Feb 19-11:37 PM

## STANDARD Colour Code

TABLE 10-1

COLOUR	NUMERIC VALUE
Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Grey	8
White	9

Feb 19-11:46 PM

# 60 x 10 RESISTOR Colour Code

TABLE 10-2 READING RESISTOR COLOUR BANDS

COLOUR	1st NUMBER	2nd NUMBER	MULTIPLIER	TOLERANCE (PERCENT)
Black	0	0	1	
Brown	1	1	10	
Red	2	2	100	
Orange	3	3	1 000	
Yellow	4	4	10 000	
Green	5	5	100 000	
Blue	6	6	1 000 000	
Violet	7	7	10 000 000	
Gray	8	8	100 000 000	
White	9	9	1 000 000 000	
Gold			0.1	5
Silver			0.01	10
None				20
	BAND 1	BAND 2	BAND 3	BAND 4



Feb 19-11:56 PM

## Colour Code BANDS



- Read left to right
  - The colour band closest to one end of the resistor is where you start
  - First 2 colour bands represents first 2 digits in resistance value.
  - 3<sup>rd</sup> band represents multiplier
- \*The first 2 numbers are multiplied by the multiplier to obtain the actual resistance.
- when 4<sup>th</sup> band is present it represents the percentage tolerance of resistor.

\*either gold or silver  
 $\pm 5\%$      $\pm 10\%$

never see  $\pm 20\%$

Feb 19-11:47 PM

FIGURE 10-10 A, B, C

PDF File.

Step 1: Match the color bands to the number



Resistance Value	
Red	= 2
Blue	= 6

Handwritten calculation:  $26000 \times 10\%$

Step 3: Calculate the percentage value to add and subtract

total  $\Omega$  x percent as decimal or total  $\Omega$  x percent  $\div$  100

$0.10 \times 26\ 000 = 2600$

or


$26\ 000 \times 10 \div 100 = 2600$

Step 4: Calculate the high and low by adding to the total  $\Omega$

Actual High =  $26000\Omega + 2600 = 28\ 600\ \Omega$

Actual low =  $26000\Omega - 2600 = 23\ 400\ \Omega$

Feb 19-11:55 PM

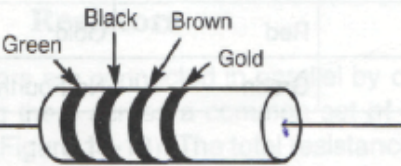

B.

Resistance Value

Green	= 5
Black	= 0
Brown	= $\times 10$
Gold	= $\pm 5\%$ tolerance
$\therefore$ Resistance Value is $500\ \Omega \pm 5\%$	
(actual resistance value may vary 25 $\Omega$ above or below this value)	

$0.05 \times 500 = 25$

Actual High =  $500 + 25$

Actual low =  $500 - 25$

525  $\Omega$

475  $\Omega$


Handwritten calculation:  $500 \pm 25$

Handwritten boxes for tolerance range:  $475$  to  $525$


Feb 20-12:01 AM


Resistance Value


Yellow = 4  
 Violet = 7  
 Black = 0  
 No Fourth Band =  $\pm 20\%$   
 $\therefore$  Resistance Value is  $47 \pm 20\%$

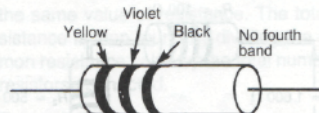c. 

$47 \times 1 = 47 \Omega$


  $0.2 \times 47 = 9.4$


Actual High =  $47 \Omega + 9.4$   
  $56.4 \Omega$


Actual low =  $47 \Omega - 9.4$   
  $37.6 \Omega$


6


Feb 20-12:05 AM

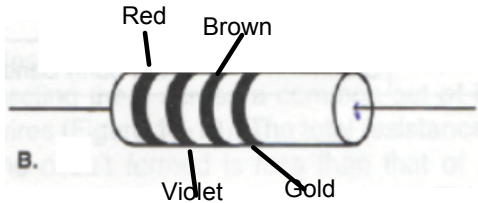
1 

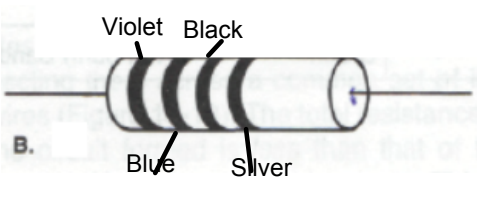2 

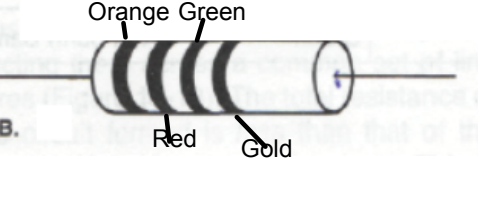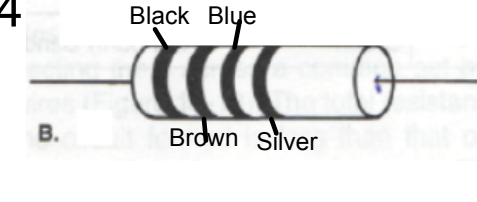
3 

4 

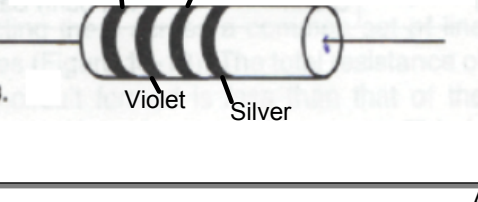5 

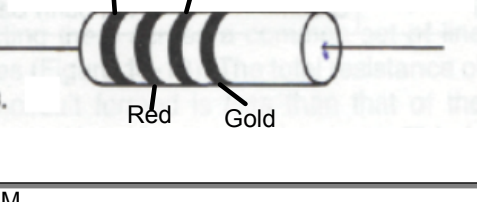6 

Apr 30-8:37 AM

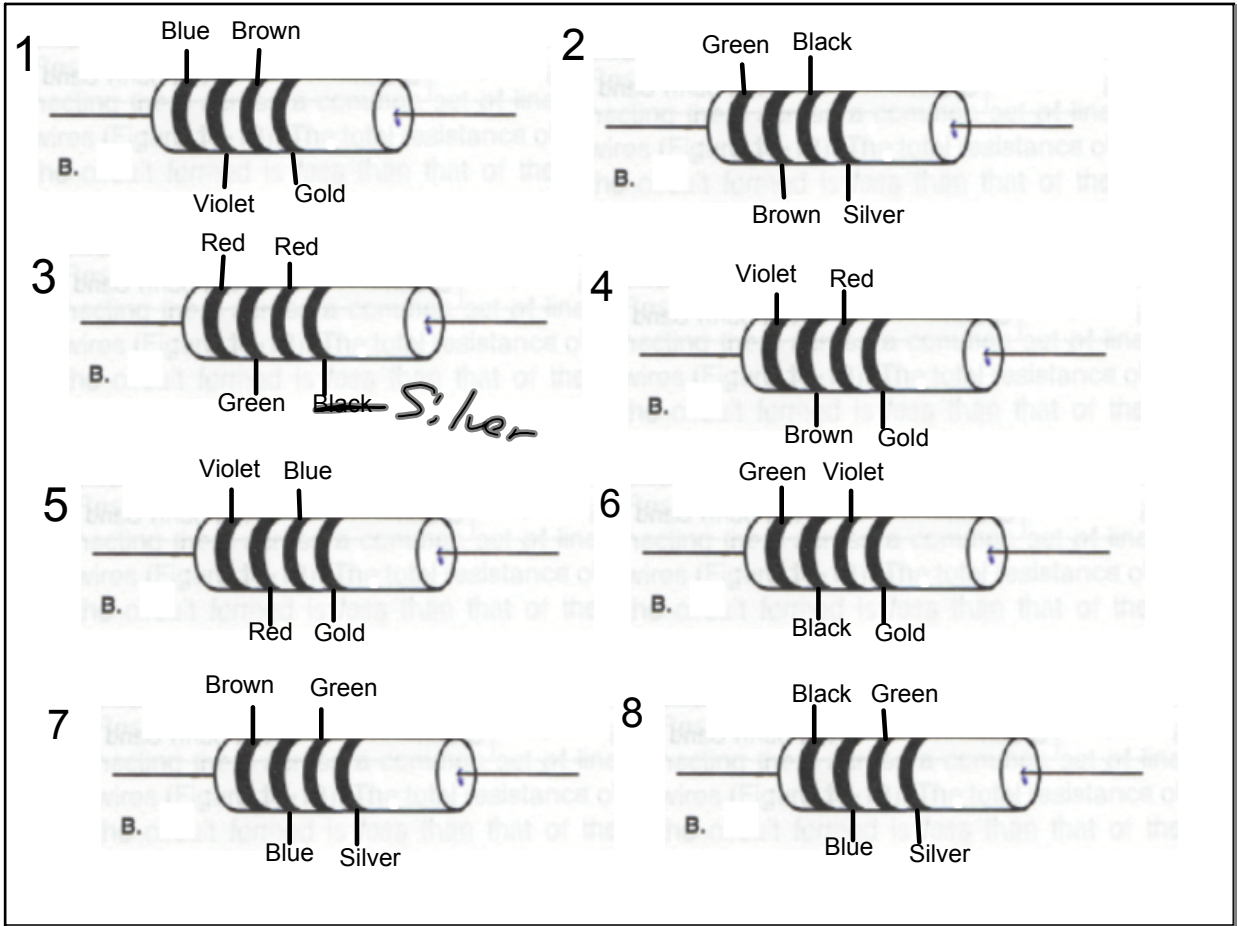

May 5-9:13 AM

1. Blk - 6	67 x 10
Violet - 7	670 ± 5%
Brown - 10	670 ± 5%
Gold - 5%	670 ± 33%
	Max - 702.5 Ω
	Min - 637.5 Ω
2. Green - 5	51 x 1
Brown - 1	51 ± 10%
Black - 1	51 ± 10%
Silver - 10%	51 ± 5%
	Max - 56.1
	Min - 45.7
3. Red - 2	25 x 100
Green - 5	2500 ± 10%
Red - 100	2500 ± 250
Silver - 10%	Max - 2750 Ω
	Min - 2250 Ω
4. Violet - 7	71 x 100
Brown - 1	7100 ± 5%
Red - 100	7100 ± 35%
Gold - 5%	Max - 746.5 Ω
	Min - 673.5 Ω
5. Violet - 7	72 x 1000000
Red - 2	72000000 ± 5%
Blk - 6	72000000
Gold - 5%	Max - 75600000
	Min - 68400000
6. Green - 5	50 x 1000000
Black - 0	50000000
Violet - 7	50000000
Gold	50000000 ± 5%
	Max 52500000
	Min 47500000
7. Brown - 1	16 x 10000
Blk - 6	160000 ± 10%
Green - 100000	160000 ± 10%
Silver - 10%	Max - 176000
	Min - 144000
8. Black - 0	6 x 100000
Blk - 6	600000 ± 10%
Green - 100000	600000 ± 10%
Silver - 10%	Max - 660000
	Min - 540000

May 5-2:36 PM

Step 1: Match the color bands to the number




Step 3: Calculate the percentage value to add and subtract

Step 4: Calculate the high and low by adding to the total  $\Omega$

Apr 21-6:54 PM

You Try

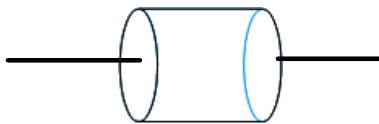

$$6\,100\,000\Omega \times 0.2 = 1\,220\,000\Omega$$

OR

$$6.1\text{ M}\Omega \times 0.2 = 1.22\text{ M}\Omega$$



Actual High

$$6\,100\,000\Omega + 1\,220\,000\Omega = 7\,320\,000\Omega$$

or

$$7.23\text{ M}\Omega$$



### Resistance Value

blue = 6

brown = 1

green =

NO Fourth Band =

$\therefore$  Resistance Value is



$$6\,100\,000\Omega \pm 20\%$$

OR

$$6.1\text{ M}\Omega \pm 20\%$$

Actual Low

$$6\,100\,000\Omega - 1\,220\,000\Omega = 4\,880\,000\Omega$$

or

$$4.88\text{ M}\Omega$$

Feb 21-7:08 PM

$\Omega - 1\Omega$   
 $K\Omega - 1000\Omega$   
 $M\Omega - 1000000\Omega$   
 $7.000000\Omega$   
 $7m\Omega$

$57.000\Omega$   
 $57K\Omega$

$4600\Omega$   
 $4.6K\Omega$


May 6-2:05 PM

-resistor values less than 10Ω will bear colour gold or silver on THIRD band

if on 3<sup>rd</sup> Band

(Figure 10-11) (A gold third band requires you to multiply the value indicated by the first two digits by 0.1. A silver third band indicates a multiplier of 0.01.)

FIGURE 10-11

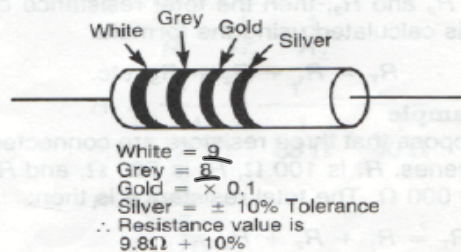

$98 \times 0.1 = 9.8\Omega$   
 $9.8 \pm 10\%$   
 $9.8 \pm 0.98$   
 $Max = 9.8 + 0.98 = 10.78\Omega$   
 $Min = 9.8 - 0.98 = 8.82\Omega$

Feb 21-7:15 PM

Use the colour code chart to determine the resistor code

TABLE 10-3

GIVEN RESISTANCE VALUE	COLOUR CODE			
	1st BAND	2nd BAND	3rd BAND	4th BAND
$360 \Omega \pm 5\%$	Orange	Blue	Brown	Gold
$10 \Omega \pm 10\%$	Brown	Black	Black	Silver
$4700 \Omega \pm 20\%$	Yellow	Violet	Red	No Fourth Band
$5 \Omega \pm 10\%$	Green	Black	Gold	Silver
$8000 \Omega \pm 5\%$	Grey	Black	Red	Gold
$3300000 \Omega \pm 20\%$	Orange	Orange	Green	No Fourth Band

S = Green  
 O = Black  
 S O x 0.1

Feb 21-7:33 PM

Units are important:

⑤  $52 \text{ K} \Omega = 52 \times 1000 = 52000 \Omega$

GIVEN RESISTANCE VALUE	COLOUR CODE			
	1st BAND	2nd BAND	3rd BAND	4th BAND
a) $52 \text{ K}\Omega \pm 5\%$	green	red	orange	gold
b) $6 \text{ M}\Omega \pm 10\%$	blue	black	green	silver
c) $3.8 \text{ K}\Omega \pm 20\%$	orange	grey	red	None

a)  $52 \text{ K}\Omega$   
 $= 52 \times 10^3 \Omega$   
 $= 52000 \Omega$   
 digit 1 = 5 green  
 digit 2 = 2 red  
 multiplier = 1000 orange

b)  $6 \text{ M}\Omega$   
 $= 6 \times 10^6 \Omega$   
 $= 6000000 \Omega$   
 digit 1 = 6 blue  
 digit 2 = 0 black  
 multiplier = 100000 green


c)  $3.8 \text{ K}\Omega$   
 $= 3.8 \Omega \times 10^3$   
 $= 3800$   
 digit 1 = 3 orange  
 digit 2 = 8 grey  
 multiplier = 100 red

Feb 21-7:43 PM



Ex) Determine the resistor code

Blue Green Red

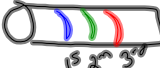

Step 1) Match colors to numbers

- 1) Blue = 6
- 2) Green = 5
- 3) Red =  $\times 100$
- 4) None = 20%

2 digit

$65 \times 100 \Omega \pm 20\%$

Step 2)  $R_1 = 6500 \Omega \pm 20\%$

Step 3)

$0.20 \times 6500 \Omega = 1300 \Omega$

<p>High (+)</p> $6500 \Omega + 1300 \Omega$ $7800 \Omega$		<p>Low (-)</p> $6500 \Omega - 1300 \Omega$ $5200 \Omega$
---	--	--

Apr 23-1:56 PM

Ex) Determine the resistor code

Blue Gray Silver Silver

$68 \times 0.01 \pm 10\%$

$0.68 \Omega \pm 10\%$

Apr 23-1:59 PM

Ex)  $56 \text{ M}\Omega \pm 5\%$  $\times 1,000,000$  $56,000,000 \Omega \pm 5\%$ 

green blue blue gold

$$1 \text{ k}\Omega = 1000 \Omega$$

$$1 \text{ M}\Omega = 1,000,000 \Omega$$

$$7 \text{ k}\Omega \pm 20\%$$

Change to  $\Omega$   
 $\times 1000$ 

$$7,000 \Omega \pm 20\%$$

Violet black Red

Apr 23-1:59 PM

Assignment On Resistor colour Code


worksheet 8 &amp; hand drawn

Feb 21-8:02 PM



## Resistor in SERIES

Recall series are connected end-to-end

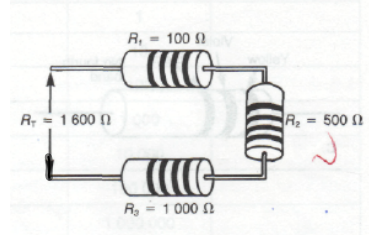


Total resistance is the sum of individual resistance.

$$\underline{R_T} = R_1 + R_2 + R_3 \text{ , etc.}$$

$$R_T = 100\ \Omega + 500\ \Omega + 1000\ \Omega$$

$$= 1600\ \Omega$$


Feb 21-8:05 PM

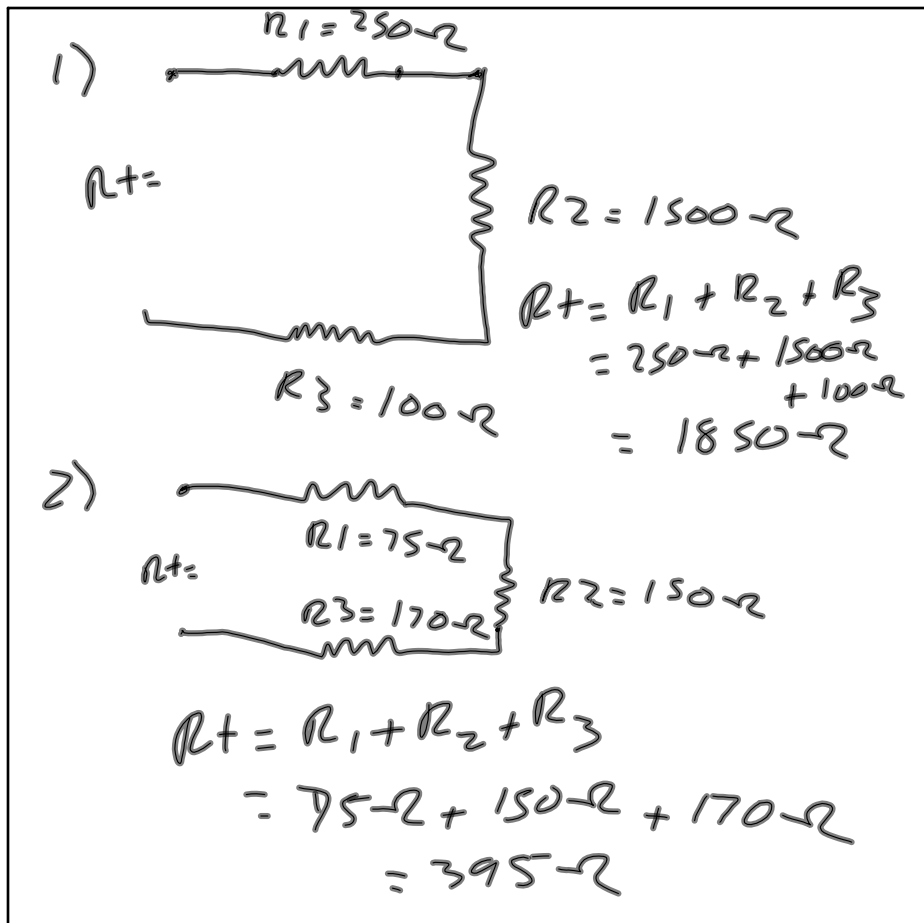

May 9-2:12 PM

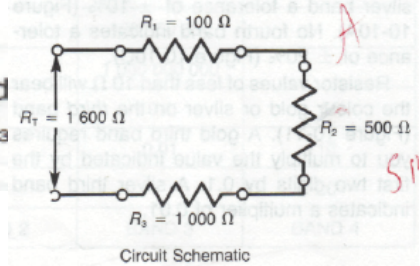**Example**

Suppose that three resistors are connected in series.  $R_1$  is  $100\ \Omega$ ,  $R_2$  is  $500\ \Omega$ , and  $R_3$  is  $1\ 000\ \Omega$ . The total resistance is then:



$$R_T = R_1 + R_2 + R_3$$

$$R_T = 100\ \Omega + 500\ \Omega + 1\ 000\ \Omega$$

$$R_T = 1\ 600\ \Omega$$

Mar 11-10:58 AM

## Resistor in Parallel Connection

Resistors are connected in parallel

Total resistance is LESS than that of the lowest resistant value.

Because each resistors provides a separate parallel path for the current flow

Total resistance is calculated using fractions.


Feb 21-8:05 PM

## Resistor in Parallel Connection

If the Resistance all have the same value then,

Total resistance is calculated using fractions.

$$R_T = \frac{R(\text{Common Value})}{\text{number of resistors}} = \frac{75 \Omega}{3} = 25 \Omega$$

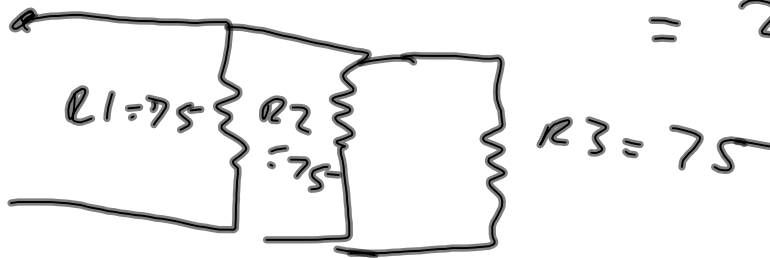


Feb 21-8:05 PM

## Resistor in Parallel Connection

All the R are the same

Example)

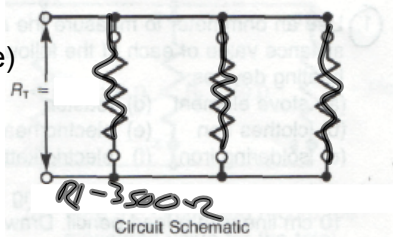


$$R_T = \frac{350 \Omega}{3} = 116.7 \Omega$$

Total resistance is calculated using fractions.

$$R_T = \frac{R(\text{Common Value})}{\text{number of resistors}}$$

**Example**


Suppose that three 150 Ω resistors are connected in parallel. The total resistance is then:

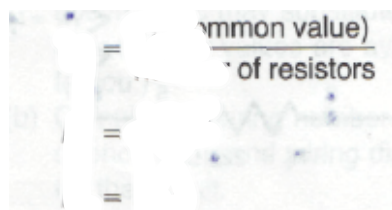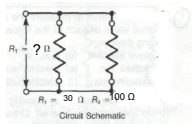

Feb 21-8:05 PM

**Resistor in Parallel Connection**  
2 Unequal Resistor Value


Total Resistance of 2 unequal values of resistors connected in parallel:

$$R_T = \frac{R_1 \times R_2}{R_1 + R_2}$$


Circuit Schematic

$$R_T = \frac{30 \times 100}{30 + 100}$$

$$= \frac{3000}{130}$$

$$= 23 \Omega$$


$$R_T = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{56 \times 1400}{56 + 1400}$$

$$= \frac{78400}{1456} = 54 \Omega$$

Feb 21-8:05 PM

- A circuit consists of 3 resistors connected in series. The resistors are 50 ohms, 75 ohms and 1500 ohms. What is the total resistance in the circuit.  

$$R_T = R_1 + R_2 + R_3 = 50 \Omega + 75 \Omega + 1500 \Omega = 1625 \Omega$$
- A circuit consists of 3 resistors connected in series. The resistors are 175 ohms, 1800 ohms and 2400 ohms. What is the total resistance in the circuit.  

$$R_T = 175 \Omega + 1800 \Omega + 2400 \Omega = 4375 \Omega$$
- A circuit consists of 3 resistors connected in parallel. The value of each resistor is 750 ohms. What is the total resistance of the circuit?  

$$R_T = \frac{\text{Sum of Values}}{3} = \frac{2250 \Omega}{3} = 750 \Omega$$
- A Circuit contains 3 resistors connected in parallel. R1 has a value of 150 ohms, R2 has a value of 1300 Ohms, and R3 has a value of 65 ohms. What is the total resistance in the circuit.
- A circuit contains 2 resistors connected in parallel. R1 has a value of 3500 ohms, and R2 has a value of 500 ohms. What is the total resistance of the circuit.  

$$R_T = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{3500 \times 500}{3500 + 500}$$

$$= \frac{1750000 \Omega}{4000 \Omega}$$


$$= 437.5 \Omega$$

May 12-1:39 PM

## Resistor in Parallel Connection

### 2 Unequal Resistor Value

Example) Suppose that a  $60\ \Omega$  resistor is connected in parallel with one of  $40\ \Omega$ . The total resistance is then:

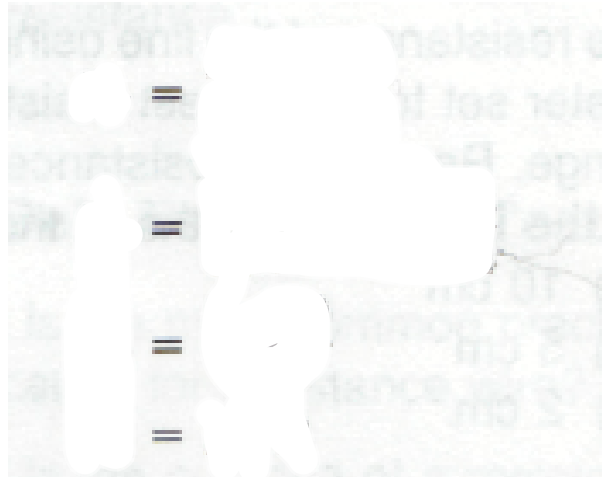


Feb 21-8:05 PM

## Resistor in Parallel Connection
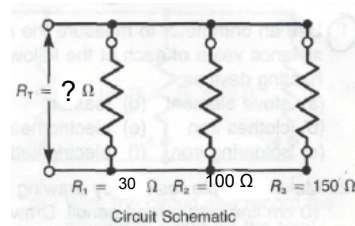
### 3 or more Unequal Resistor Value

Total Resistance of 3 unequal values of resistors connected in parallel:

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$



$$R_T = \frac{1}{\frac{1}{30} + \frac{1}{100} + \frac{1}{150}}$$

$$= \frac{1}{0.033 + 0.01 + 0.0067}$$

$$= \frac{1}{0.050} = 20\ \Omega$$

Feb 21-8:05 PM

4. A Circuit contains 3 resistors connected in parallel. R1 has a value of 150 ohms, R2 has a value of 1300 Ohms, and R3 has a value of 65 ohms. What is the total resistance in the circuit.

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$R_T = \frac{1}{\frac{1}{150} + \frac{1}{1300} + \frac{1}{65}}$$

$$R_T = \frac{1}{0.0067 + 0.00077 + 0.015}$$

$$R_T = \frac{1}{0.02247}$$

$$= 44.5$$

$$= 45 \Omega$$

May 12-2:20 PM

## Resistor in Parallel Connection

3 or more Unequal Resistor Value

### Example

Suppose that a 120  $\Omega$ , 60  $\Omega$ , and 40  $\Omega$  resistor, are all connected in parallel. The total resistance is then:

Mar 11-11:00 AM



1. A circuit consists of 3 resistors connected in series. The resistors are 3600 ohms, 7500 ohms and 1100 ohms. What is the total resistance in the circuit.

$$R_T = R_1 + R_2 + R_3 = 3600\text{-}\Omega + 7500\text{-}\Omega + 1100\text{-}\Omega = 12.2\text{ k}\Omega = 12200\text{-}\Omega + 1100\text{-}\Omega$$

2. A circuit consists of 3 resistors connected in series. The resistors are 1750 ohms, 100 ohms and 2200 ohms. What is the total resistance in the circuit.

$$R_T = R_1 + R_2 + R_3 = 1750\text{-}\Omega + 100\text{-}\Omega + 2200\text{-}\Omega = 4050\text{-}\Omega = 4.1\text{ k}\Omega$$

3. A circuit consists of 3 resistors connected in parallel. The value of each resistor is 1350 ohms. What is the total resistance of the circuit?

$$R_T = \frac{\text{Common Value}}{\# \text{ Resistors}} = \frac{1350}{3} = 450\text{-}\Omega$$

4. A circuit contains 3 resistors connected in parallel. R1 has a value of 15 ohms, R2 has a value of 13 Ohms, and R3 has a value of 16 ohms. What is the total resistance in the circuit.


$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{1}{15} + \frac{1}{13} + \frac{1}{16}}$$


5. A circuit contains 2 resistors connected in parallel. R1 has a value of 3100 ohms, and R2 has a value of 7500 ohms. What is the total resistance of the circuit.

$$R_T = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{3100 \times 7500}{3100 + 7500} = \frac{23,250,000}{10600} = 2193\text{-}\Omega = 2.2\text{ k}\Omega$$

May 12-2:18 PM


Unit 10 Assignment

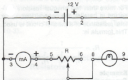1)  a) Complete the number sequence chart for the above diagram.

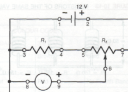2)  a) Complete the number sequence chart for the above diagram.


3) Write out 10 resistor codes and their corresponding color bands.

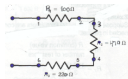4) a) Calculate the total resistance of the below diagram.




b) Complete the number sequence chart for the above diagram.

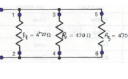
5) a) Calculate the total resistance of the below diagram.



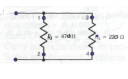6) a) Calculate the total resistance of the below diagram.



7) a) Calculate the total resistance of the below diagram.

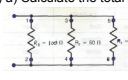

Mar 12-11:32 AM

# Questions 1 - 11

Page 99

## Self Evaluation

I will chooses some

(1,2,4,5,6,7,8,10,11(all))

# Hand in

Mar 11-11:43 AM

May 12-8:35 AM