 


Unit 12
Solving The Series
Circuit


Jan 29-10:29 AM



Series Circuit Connection

- Recall series are connected end-to-end
- Only one pathway can be traced from one side of the voltage source to the other.
 - one path for electrons to travel
 - If path gets broken anywhere then current flow stops (doesn't work anymore)


FIGURE 12-1 SERIES CIRCUIT

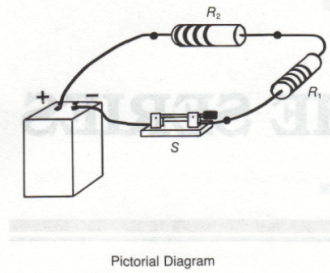

Mar 14-10:53 AM

When we have more than one load resistor we use subscripts to identify the difference in the circuit quantities.

Current	I_1, I_2, I_3, \dots	Individual current across each resistor
Voltage	V_1, V_2, V_3, \dots	Individual voltage drop across each resistor
Resistance	R_1, R_2, R_3, \dots	Individual resistors

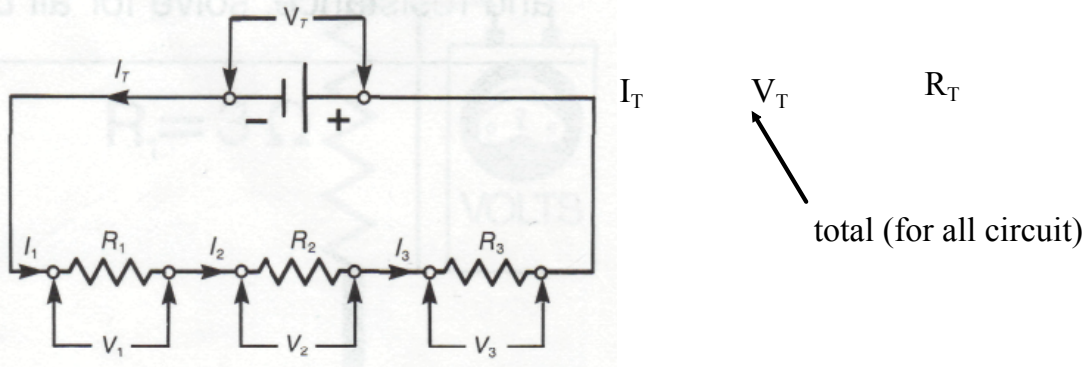


Mar 14-11:21 AM

Series Circuit: Current

Current is the **SAME** throughout a **SERIES**

$$I_T = \underline{I_1} = \underline{I_2} = \dots$$

FIGURE 12-3 THE CURRENT IS THE SAME AT ALL POINTS IN A SERIES CIRCUIT

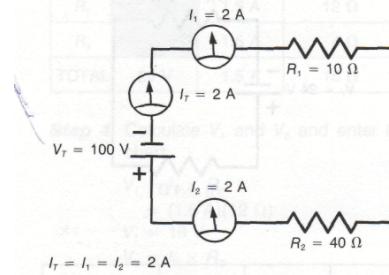


- Because there is only one path. There is no loss or gain of current.

* e⁻ flow out from negative side of voltage source and **MUST** flow through each component and return to the positive side of the voltage source

Mar 15-11:11 AM

FIGURE 12-3 THE CURRENT IS THE SAME AT ALL POINTS IN A SERIES CIRCUIT

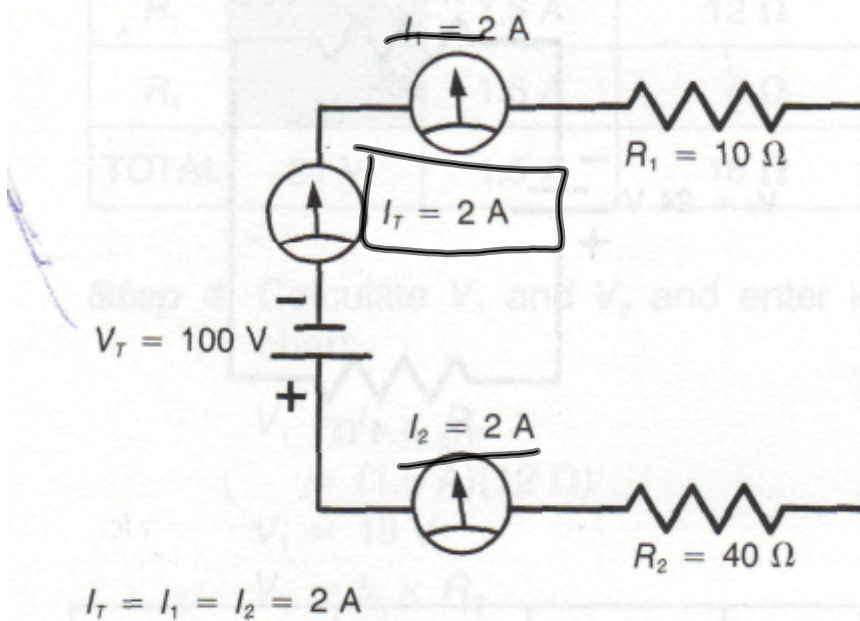


May 21-2:18 PM


Series Circuit: Voltage

- Voltage in a series circuit is divided among each of the loads
- Amount depends on the resistance value on the load (Directly proportional)
- **Total Voltage Drop**: is the sum of individual voltage drops

$$V_T = V_1 + V_2 + V_3 \dots$$

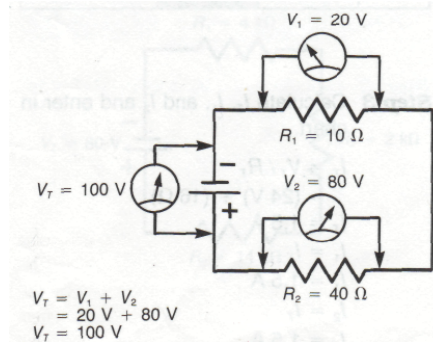

Mar 15-11:25 AM

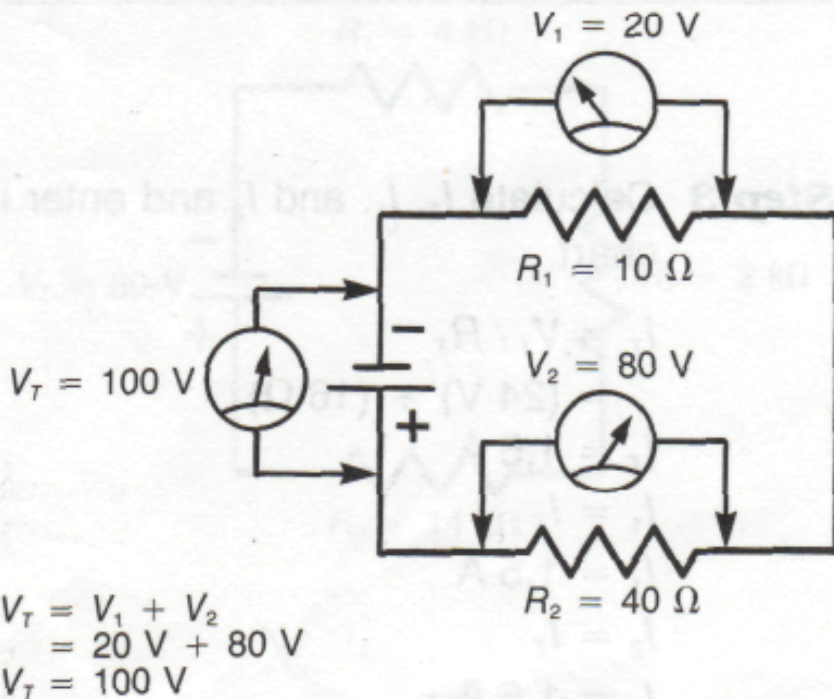


May 21-2:28 PM

Series Circuit: Resistance

- **Total Resistance**: is the sum of individual load resistors

- Because there is only one path for e⁻ to flow they **MUST** travel through each load resistor.

$$R_T = R_1 + R_2 + R_3 \dots$$

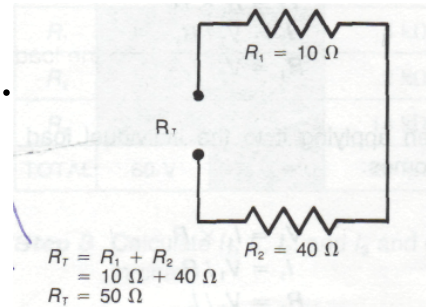

Mar 15-11:26 AM

Solving Series Circuits



- Calculating unknown values when give at least 2 other values

Will need to use:

$$\underline{V = IR}$$

$$\underline{R = \frac{V}{I}}$$

$$\underline{I = \frac{V}{R}}$$

And

$$I_T = I_1 = I_2 = \dots$$

$$R_T = R_1 + R_2 + R_3 \dots$$

$$V_T = V_1 + V_2 + V_3 \dots$$

Mar 15-11:39 AM

Solving Series Circuits as a WHOLE

$$V_T = \underline{I_T} \times R_T$$

$$R_T = \frac{V_T}{I_T}$$

$$I_T = \frac{V_T}{R_T}$$

Mar 17-5:32 PM

Solving Series Circuits as an INDIVIDUAL

$$V_1 = I_1 \times R_1$$

$$R_1 = \frac{V_1}{I_1}$$

$$I_1 = \frac{V_1}{R_1}$$


and
so
on...

Charts
help

Mar 17-5:32 PM

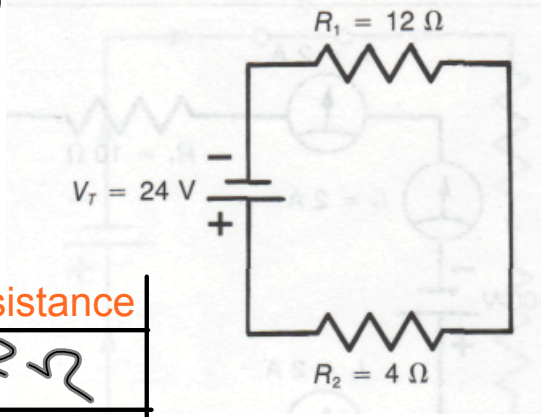Example 1)

Find all the unknown values of V, I and R for each circuit below. (SHOW ALL WORK)



Step 1) Make a chart


Resistors

	Voltage	Current	Resistance
R ₁			12 Ω
R ₂			4 Ω
Total	24V		

Mar 17-5:43 PM

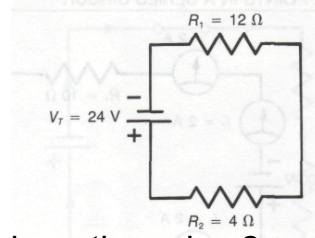Example 1) continued

Find all the unknown values of V, I and R for each circuit below. (SHOW ALL WORK)



Step 2) Fill in the information given and start where they give 2 pieces of info in the same column or row.


	Voltage	Current	Resistance
R ₁			12 Ω
R ₂			4 Ω
Total	24 V		16 Ω

} Given both R₁ & R₂ so can calculate R_T

$$R_T = R_1 + R_2$$

Mar 17-5:43 PM

Example 1) continued

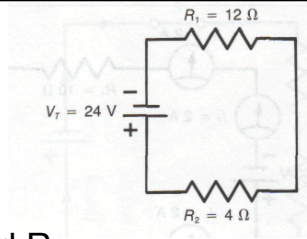


Step 3) Solve for when given R_1 and R_2 .

$$\begin{aligned} R_T &= R_1 + R_2 \\ &= 12\Omega + 4\Omega \\ &= 16\Omega \end{aligned}$$

	Voltage	Current	Resistance
R_1			12 Ω
R_2			4 Ω
Total	24 V		<u> </u> Ω

Mar 17-5:43 PM

Example 1) continued

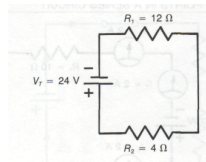

Step 4) Calculate I_T . (also I_1 and I_2 since all are equal) $I_T = I_1 = I_2 = \dots$

$$I_T = \frac{V_T}{R_T}$$

$$I_T = \frac{24\text{ V}}{16\Omega}$$

$$I_T = 1.5\text{ A}$$

	Voltage	Current	Resistance
R_1			12 Ω
R_2			4 Ω
Total	24 V	<u>1.5 A</u>	<u>16 Ω</u>

Mar 17-5:43 PM

$$I_T = I_1 = I_2 = \dots$$

	Voltage	Current	Resistance
R ₁	18V	1.5 A	12 Ω
R ₂	6V	1.5 A	4 Ω
Total	24 V	1.5 A	16 Ω

OP
love


Now can calculate Voltage 1 and Voltage 2

$$\begin{aligned} V_1 &= I_1 \times R_1 \\ &= 1.5 \times 12 \\ &= 18V \end{aligned}$$

$$\begin{aligned} V_2 &= I_2 \times R_2 \\ &= 1.5 \times 4 \\ &= 6V \end{aligned}$$

Mar 17-5:55 PM


Example 1) continued	Voltage	Current	Resistance
R ₁		1.5 A	12 Ω
R ₂		1.5 A	4 Ω
Total	24 V	1.5 A	16 Ω

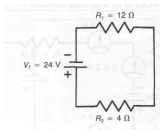

Step 5) Calculate V₁ and V₂.

$$\begin{aligned} V_1 &= I_1 \times R_1 \\ &= (1.5 \text{ A}) \times (12 \Omega) \\ &= 18 \text{ V} \end{aligned}$$


$$\begin{aligned} V_2 &= I_2 \times R_2 \\ &= (1.5 \text{ A}) \times (4 \Omega) \\ &= 6 \text{ V} \end{aligned}$$



	Voltage	Current	Resistance
R ₁	V	A	12 Ω
R ₂	V	A	4 Ω
Total	24 V	A	Ω

DONE

Mar 17-5:43 PM

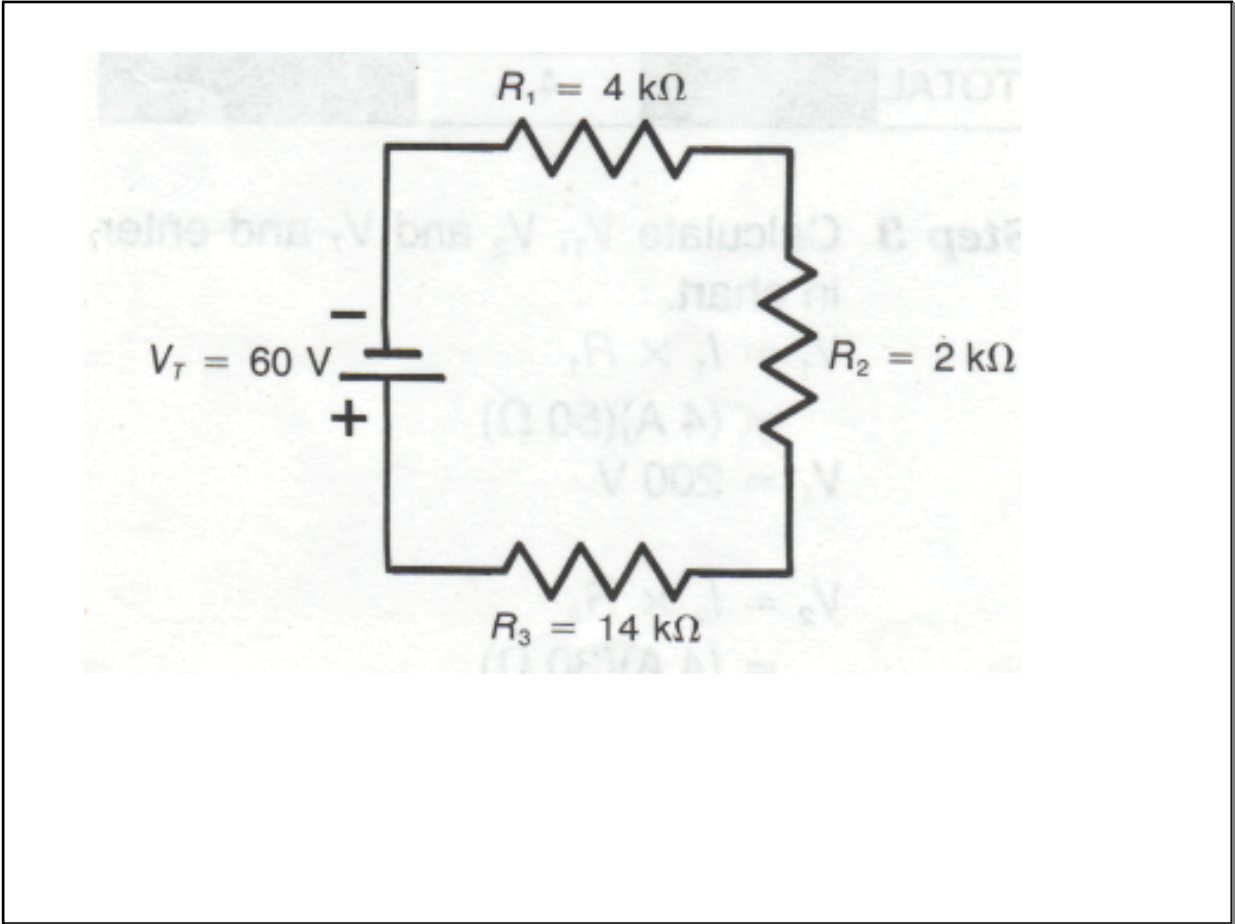


May 22-2:04 PM

Example 2) [Watch Units]

Find all the unknown values of V, I and R for each circuit below. (SHOW ALL WORK)

CHANGE ALL UNITS TO BEGIN

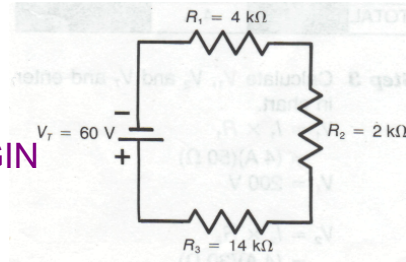

Step 1) Make a chart


	Voltage	Current	Resistance
R ₁			
R ₂			
R ₃			
Total			

Mar 17-6:12 PM

Example 2) [Watch Units]

Find all the unknown values of V, I and R for each circuit below. (SHOW ALL WORK)

CHANGE ALL UNITS TO BEGIN

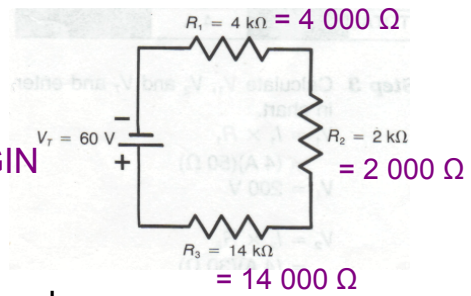

Step 2) Make a chart and fill in given numbers

	Voltage	Current	Resistance
R ₁			4 000 Ω
R ₂			2 000 Ω
R ₃			14 000 Ω
Total	60 V		

Mar 17-6:12 PM

Example 2) [Watch Units]

Find all the unknown values of V, I and R for each circuit below. (SHOW ALL WORK)

	Voltage	Current	Resistance
R ₁			4 000 Ω
R ₂			2 000 Ω
R ₃			14 000 Ω
Total	60 V		

Step 3) Calculate R_T

$$R_T = R_1 + R_2 + R_3 \dots$$

$$R_T = 4\,000\ \Omega + 2\,000\ \Omega + 14\,000\ \Omega$$

$$R_T = 20\,000\ \Omega$$

	Voltage	Current	Resistance
R ₁			4 000 Ω
R ₂			2 000 Ω
R ₃			14 000 Ω
Total	60 V		20 000 Ω

Mar 17-6:12 PM

Example 2) [Watch Units]

	Voltage	Current	Resistance
R ₁			4 000 Ω
R ₂			2 000 Ω
R ₃			14 000 Ω
Total	60 V		20 000 Ω

Step 4) Calculate I_T

$$I_T = \frac{V_T}{R_T}$$

$$I_T = \frac{60 \text{ V}}{20\,000\Omega}$$

$$I_T = 0.003 \text{ A}$$

$$I_T = I_1 = I_2 = \dots$$

	Voltage	Current	Resistance
R ₁			4 000 Ω
R ₂			2 000 Ω
R ₃			14 000 Ω
Total	60 V	0.003 A	20 000 Ω

Mar 17-6:12 PM

$$I_T = I_1 = I_2 = \dots$$

	Voltage	Current	Resistance
R ₁		0.003 A	4 000 Ω
R ₂		0.003 A	2 000 Ω
R ₃		0.003 A	14 000 Ω
Total	60 V	0.003 A	20 000 Ω

Now calculate V₁, V₂ and V₃.

Mar 17-6:24 PM

	Voltage	Current	Resistance
R ₁		0.003 A	4 000 Ω
R ₂		0.003 A	2 000 Ω
R ₃		0.003 A	14 000 Ω
Total	60 V	0.003 A	20 000 Ω

Step 5) Calculate V₁, V₂ and V₃.

$$V_1 = I_1 \times R_1$$

$$= (0.003A) \times (4000\Omega)$$

$$= 12 V$$

$$V_2 = I_2 \times R_2$$

$$= (0.003A) \times (2000 \Omega)$$

$$= 6 V$$

$$V_3 = I_3 \times R_3$$

$$= (0.003A) \times (14000\Omega)$$

$$= 42 V$$

Final Answer

	Voltage	Current	Resistance
R ₁	12 V	0.003 A	4 000 Ω
R ₂	6 V	0.003 A	2 000 Ω
R ₃	42 V	0.003 A	14 000 Ω
Total	60 V	0.003 A	20 000 Ω

Mar 17-6:35 PM

OR with more representative units

Final Answer


	Voltage	Current	Resistance
R ₁	12 V	3 mA	4 kΩ
R ₂	6 V	3 mA	2 kΩ
R ₃	42 V	3 mA	14 kΩ
Total	60 V	3 mA	20 kΩ

Mar 17-9:16 PM

You Try

Example 3)

Find all the unknown values of V, I and R for each circuit below. (SHOW ALL WORK)

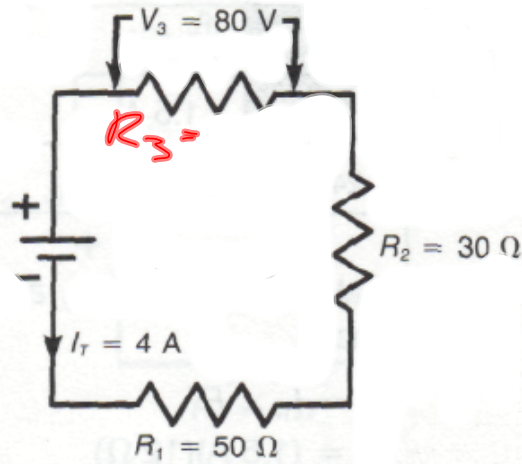

Mar 17-9:18 PM

Solution:

Step 1 Make a chart and record all known values.

	VOLTAGE	CURRENT	RESISTANCE
R_1			50 Ω
R_2			30 Ω
R_3	80 V		
TOTAL		4 A	

Step 2 Calculate I_1 , I_2 and I_3 and enter in chart.

$$I_T = I_1 = I_2 = I_3 = 4 \text{ A}$$

	VOLTAGE	CURRENT	RESISTANCE
R_1		4 A	50 Ω
R_2		4 A	30 Ω
R_3	80 V	4 A	20 Ω
TOTAL		4 A	100 Ω

$$R_T = R_1 + R_2 + R_3 = 100 \Omega$$

$$R_3 = \frac{V_3}{I_3} = \frac{80 \text{ V}}{4 \text{ A}} = 20 \Omega$$

Mar 17-9:22 PM

Step 3 Calculate V_1 , V_2 and V_T and enter in chart.

$$V_1 = I_1 \times R_1 \\ = (4 \text{ A})(50 \Omega)$$

$$V_1 = 200 \text{ V}$$

$$V_2 = I_2 \times R_2 \\ = (4 \text{ A})(30 \Omega)$$

$$V_2 = 120 \text{ V}$$

$$V_T = V_1 + V_2 + V_3 \\ = (200 \text{ V}) + (120 \text{ V}) + (80 \text{ V})$$

$$V_T = 400 \text{ V}$$

	VOLTAGE	CURRENT	RESISTANCE
R_1	200 V	4 A	50 Ω
R_2	120 V	4 A	30 Ω
R_3	80 V	4 A	20 Ω
TOTAL	400 V	4 A	100 Ω

Mar 17-9:24 PM


Step 4 Calculate R_3 and R_T and enter in chart.

$$R_3 = V_3 / I_3 \\ = (80 \text{ V}) \div (4 \text{ A}) \\ R_3 = 20 \Omega$$

$$R_T = V_T / I_T \\ = (400 \text{ V}) \div (4 \text{ A}) \\ R_T = 100 \Omega$$

	CURRENT	VOLTAGE	RESISTANCE
R_1	4 A	200 V	50 Ω
R_2	4 A	120 V	30 Ω
R_3	4 A	80 V	20 Ω
TOTAL	4 A	400 V	100 Ω

Mar 17-9:25 PM

 

May 22-2:37 PM

Fill in the chart and find the missing values

$600\text{ V} = V_T$

$I_T = 3\text{ A}$

$R_2 = 60\ \Omega$ $R_3 = 30\ \Omega$

$R_1 = ?$

	Voltage	Current	Resistance
R_1	100V	3A	110 Ω
R_2	120V	3A	60 Ω
R_3	90V	3A	30 Ω
Total	600V	3A	200 Ω

$I_T = I_1 = I_2 = I_3$

$$R_T = \frac{V_T}{I_T} = \frac{600\text{V}}{3\text{A}} = 200\ \Omega$$

$$R_1 = R_T - R_2 - R_3$$

$$= 200 - 60 - 30$$

$$= 110\ \Omega$$

$$V_1 = R_1 \times I_1 \quad V_2 = I_2 \times R_2$$

$$= 110 \times 3 \quad = 3 \times 60$$

$$= 330\text{V} \quad = 180\text{V}$$

$$V_3 = R_3 \times I_3$$

$$= 30 \times 3$$

$$= 90\text{V}$$

May 22-1:19 PM

May 22-2:46 PM

Page 121 - 122

For each diagram: Calculate the missing V, I, and R values in a chart form. **Show all work.** (You don't have to do (a), (b),... just do the calculations)

1, 2, 3, 4, 5(watch the units) ---> drawings

Page 123 - 124 (Self Evaluation Test)

Show all WORK

~~# 4 to #7~~ 1-7

HAND IN ALL WORK

Mar 17-9:25 PM

	Voltage	Current	Resistance
R_1			100 Ω
R_2			150 Ω
Total	12V		

May 26-2:06 PM

--	--	--	--

May 26-2:02 PM